

# Banasthali Vidyapith

Department of Computer Science

Computer Organization and Architecture

B.Tech.(CS-A and B), III Semester, Assignment-I, 2023

- Do the following (Arithmetic operations):
    - The signed decimal number +75 equal to — in 8 bit 2's complement.
    - The 2's complement number 10000000 is equal to — in signed decimal.
    - The number 01110000 is equal to — in signed decimal.
    - Subtract  $(10000)_2$  from  $(11010)_2$  using 1's complement.
    - Subtract  $(1010100)_2$  from  $(1010100)_2$  using 2's complement.
  - Do following arithmetic operations using 7-bit 2's complement method:
    - $(+23) + (+46)$
    - $(+23) + (-46)$
    - $(-23) + (-46)$
    - $(-23) + (+46)$
  - Design the XOR Gate using a) only NAND gate b) Only NOR gate.
  - Simplify the following Boolean expression to a minimum number of literals.
    - $F1 = (BC' + A'D)(AB' + CD')$
    - $F2 = xy + x(wz + wz')$
  - Express the complement of the following functions in the sum of min-terms:
    - $F(A, B, C, D) = \sum(0, 2, 6, 11, 13, 14)$
    - $F(x, y, z) = \prod(0, 1, 2, 3, 4, 6)$
  - Determine the Canonical SOP, POS, minimal SOP, and POS expression for the following truth table. Also draw the logic diagram for each of them.
 

|            |   |   |   |   |   |   |   |   |
|------------|---|---|---|---|---|---|---|---|
| A (Input)  | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 |
| B (Input)  | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| C (Input)  | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 1 |
| Y (Output) | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 0 |
  - Find the minimal SOP and POS expression of the following using K-map.
    - $F = \sum m(1, 5, 6, 12, 13, 14) + \sum d(2, 4)$
    - $F = \sum m(1, 3, 5, 7, 9, 15) + \sum d(4, 6, 12, 13)$
    - $F(A, B, C) = \sum m(1, 2, 5, 7) + \sum d(0, 4, 6)$
    - $F(A, B, C) = \prod(0, 3, 6, 7)$
  - Design a Full adder using 3x8 Decoder.
  - Implement 16x1 MUX using 8x1 and 2x1 MUX.
  - Draw a NAND logic diagram that implements the complement of the following function:
 
$$F(A, B, C, D) = \sum(0, 1, 2, 3, 4, 8, 9, 12)$$
  - Implement the following Boolean function using
    - 16:1 MUX
    - 8:1 MUX
    - 4:1 MUX
    - 2:1 MUX
$$F(A, B, C, D) = \sum m(0, 1, 3, 4, 8, 9, 15)$$
-